

## ABSTRACT


The 3.7V 2600mAh Li-Ion battery by Tenery Corporation requires a charging DC voltage of 4.2 V. In this application, the supplied power voltage to the circuit will be 5 V, provided by the Micro USB port. The LMR10515 Buck Converter is to be used to step-down this input voltage of 5 V to an output voltage of 4.2 V so that it can be used to charge the battery. The LMR10515 should output a desired voltage with an input voltage between 3.0 V and 5.5 V. 5 V is applied to the input node of the LMR10515 evaluation board. LMR10515 output voltage is analyzed for verification of desired operation.

## THEORY

The output voltage of the LMR10515 is determined by the following equation:

$$V_{out} = 0.6(1 + R1/R2) \quad (1)$$

Where R1 and R2 are the two resistors making up the feedback voltage divider circuit, as shown in the schematic below:

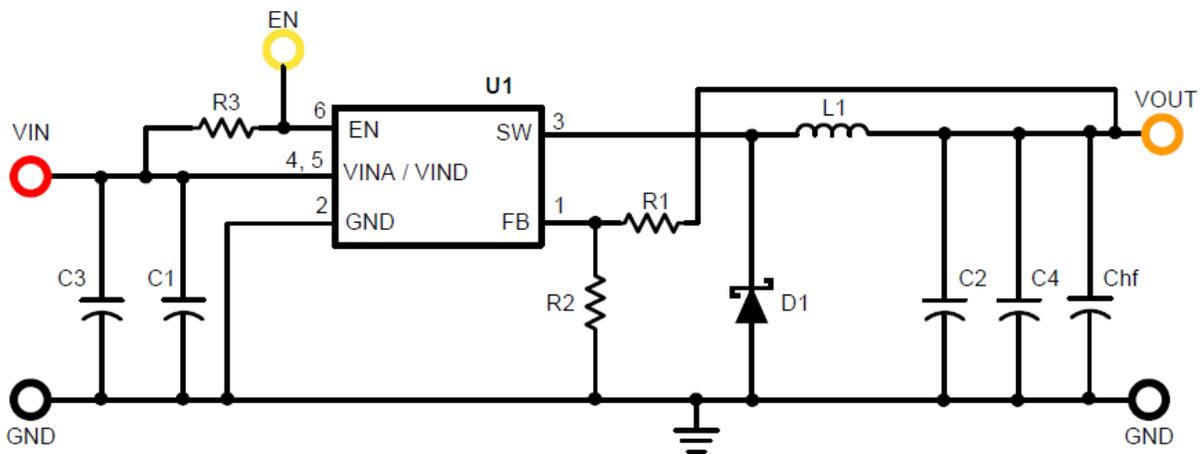

**Figure 1. LMR10515 Demo Board Schematic**

The values for R1 and R2 in the dev board used for testing are R1 = 20 kΩ and R2 = 10 kΩ. Consequently, the output voltage of the DevBoard test is expected to be 1.8 V.

## RESULTS

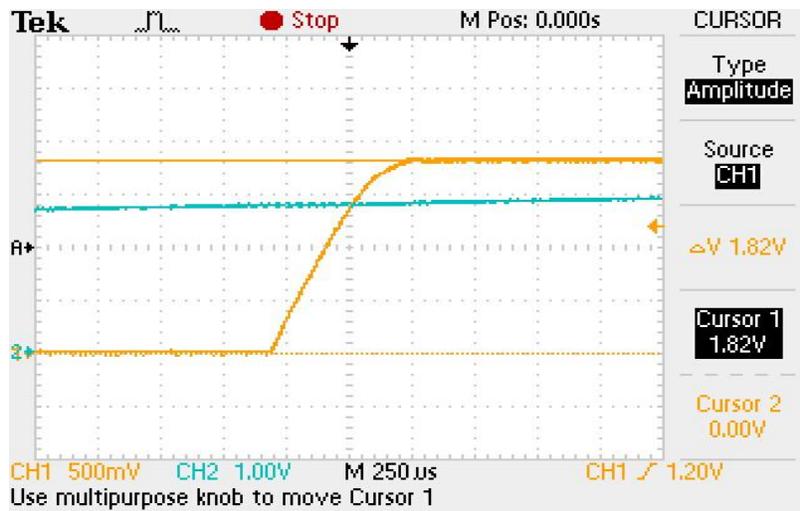


Figure 2. Input and Output Voltages of LMR10515 Dev Board when input reaches 3.0 V


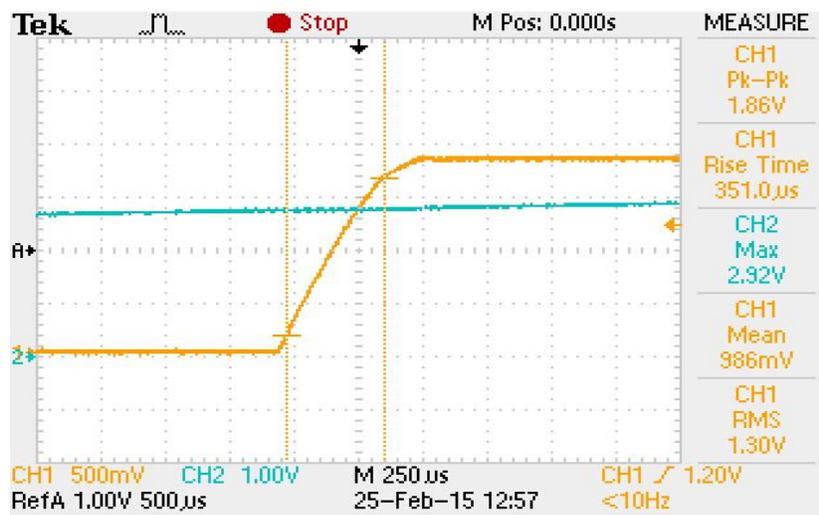


Figure 3. Timing Diagram of Figure 2; depicting output voltage rise time

Figure 2 shows the LMR10515's output voltage (orange) when its input (blue) reaches about 3.0 V. Input voltage increased 1.82 V, giving a percent error of 1.11%. Rise time of the output voltage came out to be about 351 µs.

#### CONCLUSION

Applying Equation 1 to our desired application,  $V_{out} = 4.2 V = 0.6(1 + R1/R2)$ ,  $(R1/R2) = 6$ . Keeping R1 at a resistance about six times that of R2 should provide the desired results. Application of these feedback resistors (R15 and R12) is shown in the figure below:

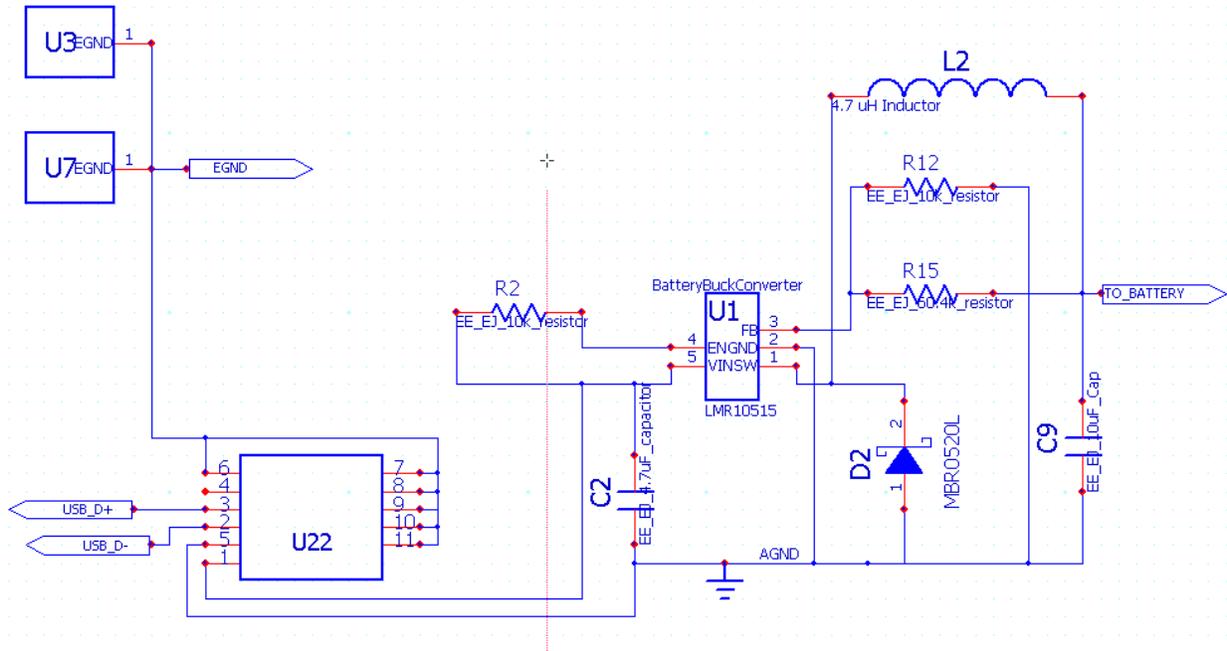

**Figure 4. Schematic Drawing of LMR10515 circuit used in PCB design**

Key Hardware Used:

LMR10515 Buck Regulator Demo Board: <http://www.ti.com/tool/LMR10515YSDDEMO>